

Regulated Tube Power Supplies

There are three schematics here.

The first is a simple one-tube supply from the 1969 GE Essential Characteristics Data Book.

I built one of these in 1969 using an old TV transformer and substituting a 5U4 for the diodes. It has been hooked to a BC-454 set to 5MHz as a WWV monitor.

The second schematic is from the same GE book. I have never built one of these, but looks like it would be a workhorse for general tube circuit design and testing.

The third schematic, inspired by the first, which I just copied from a hand-drawn schematic, is a cobbled-up supply I built for bench testing old radios (especially ex-dynamotor types). I used transformers and tubes that were plentiful in my junk box. The multiple filament transformers allows me to use 12v and 6v tubes, while avoiding the 200v cathode-to-filament limit. A third is used to provide a filament output.

The regulator tube is listed as a 6AM. That's the octal base number and includes any number of Horizontal Output tubes from TV (6BQ6, etc., I used a 12GB3). If you don't have any, you can probably get them free at your next swap meet. The 6GH8 was used as a diff-pair, simply because I have dozens of them pulled from old color TV sets. Depending upon what tube you use, this is good for about 100mA. I put the thing in a metal box as the plate cap is dangerous and the tubes get really hot.


I have versions of this where the pass-tube is replaced by a MOSFET.

I never did any analysis on this circuit, other than to paste it together. Comments are welcomed.

Have fun.

Steven Swift
Seattle, Washington
November 2005

ONE-COMPACTRON REGULATED POWER SUPPLY

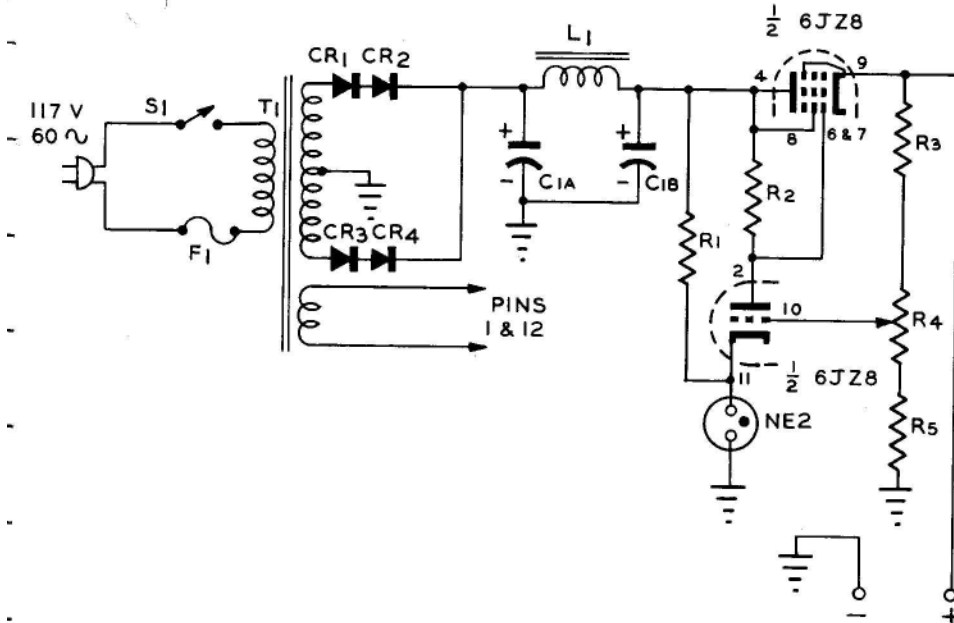

C_1 —10 μ f, 10 μ f, 450 volts

CR_1 —1N1696

CR_2 —1N1696

CR_3 —1N1696

CR_4 —1N1696

F_1 —1 ampere fuse

L_1 —8 henry, 75 milliamperes choke

R_1 —2.2 Meg.

R_2 —1 Meg.

R_3 —1 Meg.

R_4 —1 Meg. potentiometer

R_5 —470 K

S_1 —SPST toggle switch

T_1 —Power transformer: primary; 117 volts, 60 cycles; secondary 1; 6.3 volts, 3 amperes; secondary 2; 480 volts, center tapped, 70 milliamperes


Maximum Current

40 milliamperes at 150 volts

60 milliamperes at 250 volts

All resistors $\frac{1}{2}$ watt

REGULATED POWER SUPPLY

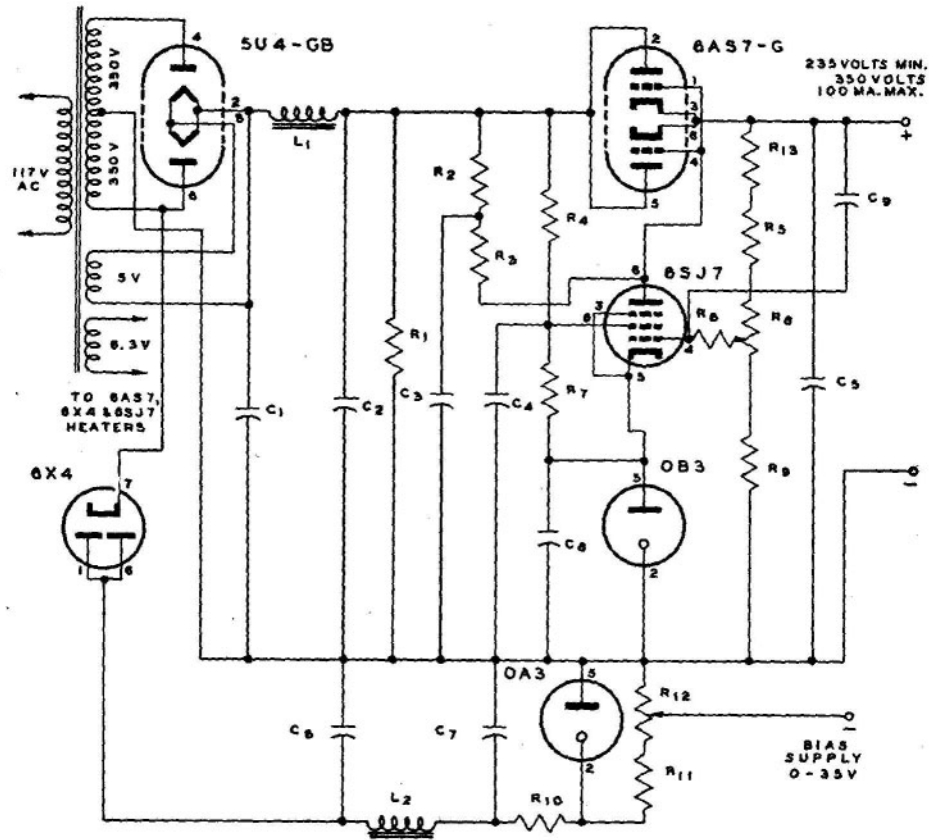


$C_1 C_2$ —16 μ f 600V
 $C_3 C_8$ —1 μ f 600V
 C_4 —8 μ f 450V
 C_5 —4 μ f 600V
 $C_6 C_7$ —40 μ f 450V
 C_9 —0.1 μ f 600V

L_1 —15 H 200 Ma
 L_2 —15 H 60 Ma
 R_1 —470 K
 $R_2 R_9 R_{12}$ —330 K
 R_3 —100 K
 R_4 —20 K 10 Watt

$R_5 R_6$ —1 Meg
 R_7 —10 K 10 Watt
 R_8 —500 K Pot.
 R_{10} —20 K 5 Watt
 R_{11} —5 K 5 Watt
 R_{12} —5 K Pot. 5 Watt

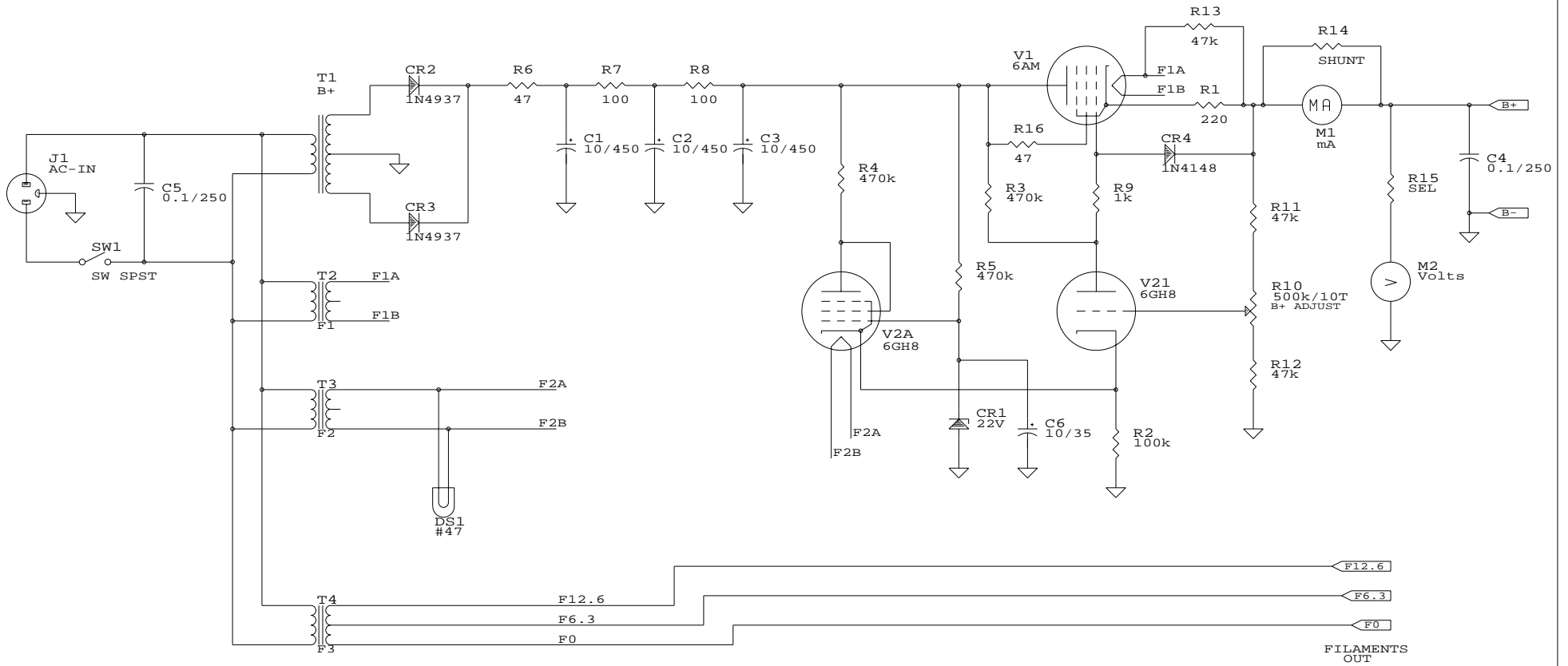All Resistors 1 Watt Unless Otherwise Specified



VARIABLE B+ BENCH SUPPLY
 USING AVAILABLE TUBES AND
 TRANSFORMERS.

pstube3.sch

Copyright 2006 Steven D. Swift, P.E.
 Seattle, Washington 98155 USA

Proprietary Information

Title		TUBE BASED BENCH SUPPLY
Size	Document Number	REV
B		-
Date:	November 5, 2005	Sheet 1 of 1